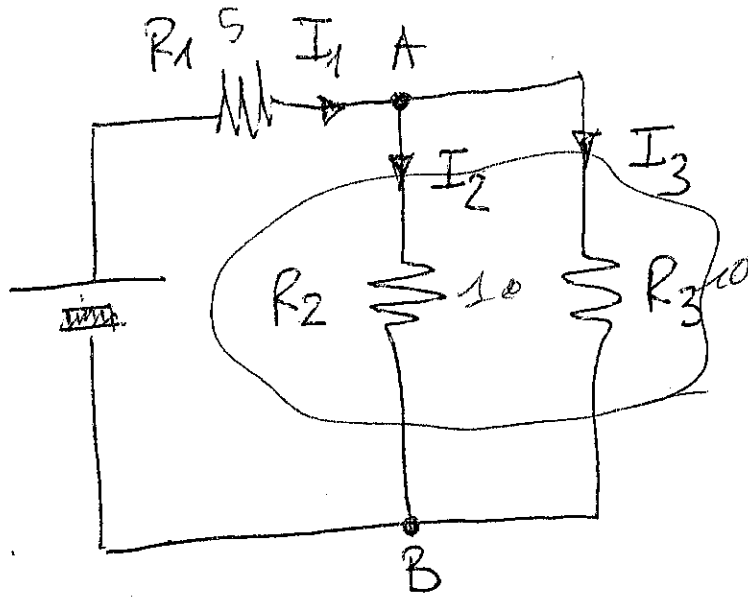


DATO IL SEGUENTE CIRCUITO

6



DATI

$$R_1 = 5 \text{ k}\Omega$$

$$R_2 = 10 \text{ k}\Omega$$

$$R_3 = 10 \text{ k}\Omega$$

$$E_1 = 10 \text{ V}$$

DETERMINARE:

La resistenza equivalente di R_2 e R_3 $5 \text{ k}\Omega$

My job is a long distance from my home, almost 50 miles away. I have to wake up early every morning, as I'm always in a rush. There's never enough time for a relaxed breakfast. At exactly 6:00 AM, I get into my car and start the long drive.